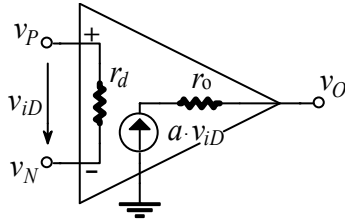


# OpAmp dc Effects and Limitations

## Low Frequency Model of OpAmp

The model contains an input differential resistance  $r_d$ , an output resistance  $r_o$  and a finite open-loop differential gain  $a$ .



$r_d$  – differential input resistance  
 $r_o$  – output resistance  
 $a$  – open-loop differential gain

Figure – OpAmp low frequency model

## Feedback in OpAmp Circuits

Typical topologies for input mixing and output sampling are presented in the next figure.

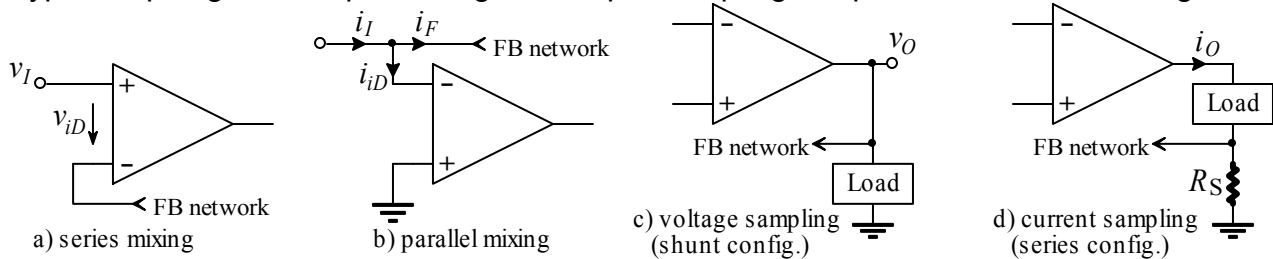


Figure – Four possible feedback topologies

Based on the OpAmp model and feedback theory the basic configuration (inverting and non-inverting amplifiers) will be analyzed

## The Non-inverting Configuration

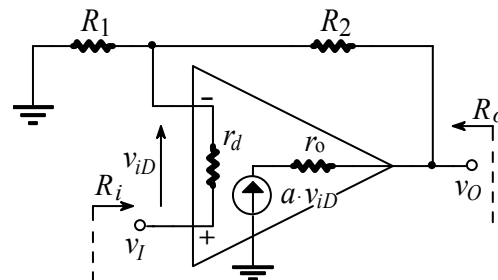


Figure – Non-inverting amplifier with the low-frequency OpAmp model

Approximate calculations of gain consider a model with ideal input and output impedances (infinite  $r_d$  and zero  $r_o$ ).

$$v_D = \frac{v_O}{a}, \quad v_N = v_I - v_D = v_I - \frac{v_O}{a} = R_1 \cdot i_1, \quad i_1 = \frac{v_I - v_O/a}{R_1}$$

$$v_O = (R_2 + R_1) \cdot i_1 = (R_2 + R_1) \frac{v_I - v_O/a}{R_1}$$

$$R_1 \cdot v_O + (R_2 + R_1) \cdot \frac{v_O}{a} = (R_2 + R_1) \cdot v_I \quad v_O \left( R_1 + \frac{R_2 + R_1}{a} \right) = (R_2 + R_1) \cdot v_I$$

$$A = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{a} + \frac{R_2}{a \cdot R_1}}$$

The feedback factor is:

$$b = \frac{v_F}{v_O} = \frac{v_N}{v_o} = \frac{R_1}{R_1 + R_2}.$$

Based on the feedback theory of the series mixing, voltage sampling configuration, the input and output impedances of the circuit are:

$$R_i \cong r_d(1 + a \cdot b) = r_d \left( 1 + a \cdot \frac{R_1}{R_1 + R_2} \right), \quad R_o \cong \frac{r_o}{1 + a \cdot b} = \frac{r_o}{1 + a \cdot \frac{R_1}{R_1 + R_2}},$$

where  $r_d$  is the input differential resistance and  $r_o$  is the output resistance of the OpAmp.

### The Inverting Configuration

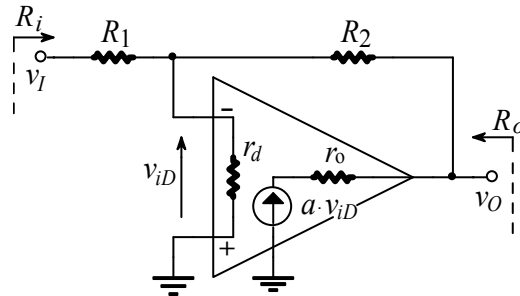


Figure – Inverting amplifier with the low-frequency OpAmp model

Same approximations of ideal input and output impedances (infinite  $r_d$  and zero  $r_o$ ) are used to simplify calculations of gain:

$$i_1 = \frac{v_I - v_D}{R_1} = \frac{v_I - v_O/a}{R_1} = i_2 = -\frac{v_O + v_O/a}{R_2}, \quad \frac{v_I}{R_1} = -\frac{1}{R_2} \left( v_O + \frac{v_O}{a} + \frac{v_O}{a} \frac{R_2}{R_1} \right),$$

$$A = \frac{v_O}{v_I} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{a} + \frac{R_2}{a \cdot R_1}}$$

The input impedance in the inverting terminal of the OpAmp  $R_n$  is affected by a shunt mixing feedback:

$$R_n = \frac{R_2 + r_o}{1 + a \cdot b} = \frac{R_2 + r_o}{1 + a \cdot \frac{R_1}{R_1 + R_2}}.$$

The circuit input and output impedances are:

$$R_i = R_1 + \frac{R_2 + r_o}{1 + a \cdot \frac{R_1}{R_1 + R_2}} \quad \text{and} \quad R_o \cong \frac{r_o}{1 + a \cdot b} = \frac{r_o}{1 + a \cdot \frac{R_1}{R_1 + R_2}}.$$

The amplifier parameters ( $A$ ,  $R_i$  and  $R_o$ ) are very closed to the ideal case for both inverting and non-inverting configuration.

## Offset Voltage and Currents

In practice a dc offset voltage can be measured at the output terminal even when the dc input voltage is zero.

The total output offset voltage can be considered to be a function of two separate effects:

- input offset voltage and
- input bias currents.

Both of the two effects are referred to the input (and measured at the output).

Both input terminals must have a dc path to the ground; such are dc connection to the output or dc path through a grounded source.

## Offset Circuit Model

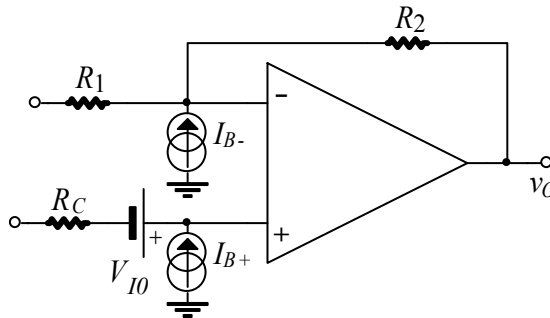


Figure – Offset circuit model – ideal sources connected to an ideal OpAmp

$V_{I0}$  – input offset voltage

$I_{B+}$  – input bias current at the non-inverting input

$I_{B-}$  – input bias current at the inverting input

The directions at the current sources are arbitrary as long as both have the same directions.

The effect of the input offset voltage at the output can be either positive or negative at a given time, so that direction of  $V_{I0}$  is arbitrary.

The basis for the offset analysis is the principle of superposition.

## Input Offset Voltage

The effect of  $V_{I0}$  at the output will be  $V_{O1}$ . This output voltage is computed (based on superposition) with all other independent sources set to zero:

- bias current sources  $I_{B+}$  and  $I_{B-}$  will be omitted (current sources set to zero),
- circuit inputs will be grounded (voltage signal sources set to zero).

The circuit that remains is the basic non-inverting amplifier and its output is:

$$|V_{O1}| = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{I0}$$

The actual output can be this value or its negative.

## Input Bias Currents

The effect of  $I_{B+}$  at the output will be  $V_{O2+}$ . The non-inverting input voltage produced by the bias current at this input over the resistance  $R_C$  is:  $R_C I_{B+}$  and the corresponding output is:

$$|V_{O2+}| = R_C I_{B+} \left( 1 + \frac{R_2}{R_1} \right)$$

The direction of the offset produced by  $I_{B+}$  will always be opposite to that of the  $I_{B-}$ :

$$|V_{O2-}| = -R_2 I_{B-}$$

The current through  $R_1$  is zero because the voltage over this resistor ( $v_N$ ) is zero (the inverting terminal is a virtual ground).

Both input bias currents effect at the output is:

$$|V_{O2}| = \left| R_C \left( 1 + \frac{R_2}{R_1} \right) I_{B+} - R_2 I_{B-} \right|$$

With an initial assumption that the two bias currents are approximate equal:

$$I_{B+} = I_{B-} = I_B,$$

the cancellation of the terms inside the magnitude bars (absolute value bars) can be achieved for:

$$|V_{O2}| = \left| R_C \left( 1 + \frac{R_2}{R_1} \right) I_B - R_2 I_B \right| = 0.$$

This will give the compensation resistor value that reduces to zero the offset component produced at the output by identical bias currents:

$$R_C = \frac{R_1 R_2}{R_1 + R_2}.$$

If the bias currents are not equal and with an optimum  $R_C$ , the output offset is:

$$|V_{O2}| = R_2 |I_{B+} - I_{B-}| \quad \text{for } R_C = R_1 \parallel R_2.$$

### **Input Offset Current**

The bias current difference term from the previous relationship appears so frequently that it is assigned a unique definition; that is the input offset current  $I_{I0}$ :

$$I_{I0} = |I_{B+} - I_{B-}|.$$

The input offset current is the magnitude of the difference between the bias currents at the two inputs. The magnitude of the output voltage offset produced by bias currents with an optimum value of compensating resistance is:

$$|V_{O2}| = R_2 I_{I0} \quad \text{for } R_C = R_1 \parallel R_2.$$

### **Typical Offset Values**

The data sheet for the general purpose OpAmp with the code 741 (e.g. LM741,  $\mu$ A741) indicates offset values:

- $V_{I0}$  – typical value is 1 mV and maximum value is 5 mV;
- $I_B$  – typical value is 80 nA and maximum value is 500 nA;
- $I_{I0}$  – typical value is 20 nA and maximum value is 200 nA.

### **Null Circuit**

Most OpAmps have provisions for nulling or eliminating offset effect at a particular operation point. A variable resistance is adjusted so that the dc output level is zero.