 


## Classical Single Stage Transistor Amplifiers

The circuits will be analyzed with *ac-dc* superposition theorem.

### The Common-Emitter Amplifier

The figure presents the circuit of the classical BJT amplifier in the common-emitter (CE) configuration. That means the emitter terminal is common to the input and to the output; the emitter is connected to ground from the signal point of view (through  $C_E$ ).



The signal source is coupled to the base of the transistor through coupling capacitor  $C_B$  and the output signal at the collector is coupled to the load,  $R_L$ , through another coupling capacitor  $C_C$ .


The emitter capacitor  $C_E$  is called bypass capacitor; the signal current  $i_e$  will flow through  $C_E$  bypassing the emitter resistance  $R_E$ . These capacitors should be chosen sufficiently large so that they acts as short-circuits over the frequency range of interest (their reactance should be much lower than the resistances seen at their terminals).

### DC Analysis

The capacitors are replaced with open-circuits; it results the voltage divider bias circuit that has been analysed previously.
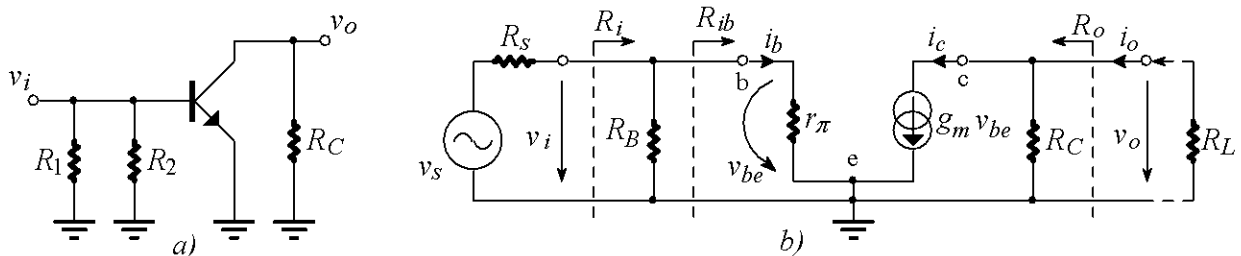
### AC Analysis

The coupling and bypass capacitors are replaced by short-circuits; the *dc* power supply is also replaced by a short-circuit. The *ac* equivalent circuit that results is presented on the left side of the next figure. For small-signal ( $v_{be} \ll V_T$ ) the transistor can be replaced by one of its small-signal model; on the right side of figure it is used the simplified hybrid- $\pi$  model.



### The open-circuit voltage gain

The voltage gain from base to collector, without load (computed with the small-signal equivalent circuit) is:

$$A_{v0} = \frac{v_o}{v_i} = \frac{-g_m v_{be} R_C}{v_{be}} = -g_m R_C$$

The minus sign in the formula indicates the phase inversion (of the output signal with respect to the input).

## The Input Impedance

The input impedance looking in the transistor base and the total input impedance seen by the signal source are:

$$R_{ib} = \frac{v_{be}}{i_b} = r_{\pi}; \quad R_i = \frac{v_i}{i_i} = R_1 \parallel R_2 \parallel R_{ib} = R_B \parallel r_{\pi}.$$

The overall voltage gain, from source to output is given by the voltage divider at the input combined with the voltage gain:

$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = A_{v0} \frac{R_i}{R_i + R_s} = -g_m R_C \frac{R_i}{R_i + R_s}.$$

## The output impedance

The output impedance is the Thevenin equivalent resistance at the output (looking from the load to the circuit with the independent source  $v_s$  suppressed):

$$v_s = 0 \Rightarrow v_{be} = 0 \Rightarrow g_m v_{be} = 0, \text{ the current source is an open-circuit and: } R_o = \left. \frac{v_o}{-i_o} \right|_{v_s=0} = R_C.$$

## Effect of Load on Voltage Gain

When a load  $R_L$  is connected to the output the collector resistance at the output is a parallel combination of the two resistances at the output and the equivalent ac collector resistance,  $R_c$ , will give the voltage gain:

$$A_v = \frac{v_o}{v_i} = -g_m R_c = -g_m (R_C \parallel R_L)$$

If one considers the voltage amplifier model, a voltage divider will be present at the output and the voltage gain (computed in a different manner) is the same:

$$A_v = A_{v0} \frac{R_L}{R_L + R_o} = -g_m R_C \frac{R_L}{R_L + R_o} = -g_m (R_C \parallel R_L).$$

The overall voltage gain (from source to load) is:

$$A_{vs} = \frac{v_o}{v_i} \frac{v_i}{v_s} = A_v \frac{R_i}{R_i + R_s} = A_{v0} \frac{R_L}{R_{RL} + R_o} \frac{R_i}{R_i + R_s} = -g_m R_C \frac{R_L}{R_L + R_o} \frac{R_i}{R_i + R_s}$$

The negative voltage gain indicates phase inversion.

## Current Gain

The overall current gain of the amplifier is given by the transistor and two current dividers:

$$A_i = \frac{i_o}{i_i} = \frac{i_o}{i_c} \frac{i_c}{i_b} \frac{i_b}{i_i} = \frac{R_c}{R_c + R_L} \beta \frac{R_B}{R_B + r_{be}} \cong \beta$$

The circuit current gain is approximately equal to the transistor current gain for:

$$R_B \gg r_{be} \text{ and } R_C \gg R_L.$$


## The Power Gain

The power gain is the product of the voltage gain and the current gain and it has a very high value (reduced by the two voltage dividers and by the two current dividers):

$$A_p = |A_v| \cdot A_i = g_m R_C \frac{R_L}{R_L + R_o} \frac{R_i}{R_i + R_s} \cdot \beta \frac{R_c}{R_c + R_L} \frac{R_B}{R_B + r_{be}}$$
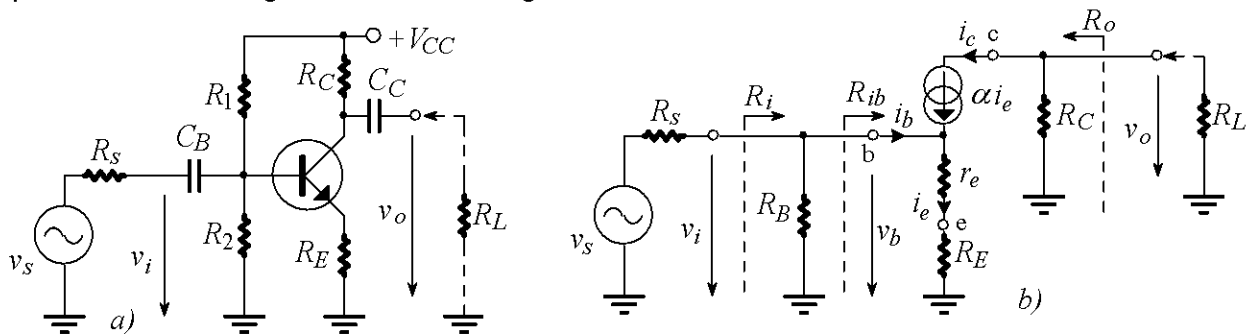
## The Common-Emitter Amplifier with Unbypassed Emitter Resistance

Leaving the emitter resistance (or part of it) unbypassed provides us with an additional design parameter that can be used to improve some performance aspects of the CE circuit at the expense of a reduction in gain. Analysis can be performed by replacing the BJT by its simplified hybrid- $\pi$  model. Let's consider the T model of BJT (ac model with  $r_e$ ); the ac equivalent circuit is given in the next figure.



## Input Resistance

Looking from the source to the amplifier you will see  $R_1$  in parallel with  $R_2$  (that is  $R_B$ ) in parallel with the input resistance looking into the base of the transistor  $R_{ib}$ :

$$R_{ib} = \frac{v_b}{i_b} = \frac{v_i}{i_b} = \frac{i_e r_e + i_e R_E}{i_e / (\beta + 1)} = (\beta + 1) \cdot (r_e + R_E); \quad R_i = R_1 \parallel R_2 \parallel R_{ib} = R_B \parallel R_{ib}$$

This first result says that: the input resistance looking into the base of a transistor is equal to the total resistance in its emitter multiplied by the factor  $(\beta + 1)$ ; that is **the reflection rule from emitter to base**.

## Voltage Gain

The voltage gain is the ratio of the total resistance in the collector to the total resistance in the emitter lead:

$$A_v = \frac{v_o}{v_i} = \frac{-\alpha \cdot i_e (R_C \parallel R_L)}{i_e (r_e + R_E)} = -\frac{\alpha \cdot (R_C \parallel R_L)}{r_e + R_E} \cong -\frac{R_C \parallel R_L}{r_e + R_E}$$


The overall voltage gain can be obtained by multiplying  $A_v$  by the transmission from the source to the input (base):

$$A_{v_s} = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = A_v \frac{R_i}{R_i + R_s} \cong -\frac{R_C \parallel R_L}{r_e + R_E} \frac{R_i}{R_i + R_s}$$

**Comparison** of the results with those of the CE amplifier indicates that leaving (part) of the emitter resistance unbypassed increases the input resistance and thus decrease the loss of signal strength in coupling the source to the amplifier input. The price paid for this improvement is a substantial reduction of voltage gain.
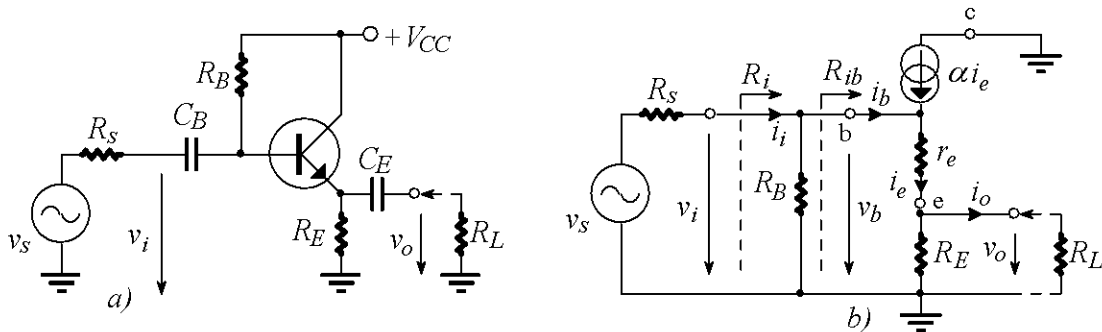
## The Emitter Follower (Common-Collector Configuration)

The emitter follower is characterized by a high input resistance and a low output resistance (compared to CE configuration). It therefore is useful as an isolated or buffer amplifier to connect a high-resistance source to a low-resistance load.



### Input Resistance

To obtain  $R_{ib}$  we use the reflection rule from emitter to base; the total resistance in the emitter lead is multiplied by  $(\beta+1)$ :

$$R_{ib} = (\beta + 1) \cdot (r_e + R_E \parallel R_L).$$

The input resistance is:

$$R_i = R_B \parallel R_{ib}.$$

### Voltage Gain

The output voltage  $v_o$  is equal to the emitter voltage and can be determined using the

voltage divider rule:

$$v_o = \frac{R_e}{R_e + r_e} v_b = \frac{R_e}{R_e + r_e} v_i;$$

With  $R_e = R_E \parallel R_L$  being the ac equivalent resistance connected at the emitter terminal.

The voltage gain is:


$$A_v = \frac{v_o}{v_i} = \frac{R_e}{R_e + r_e}. \quad A_v \cong 1 \text{ for } r_e \ll R_E.$$

The name emitter follower arises because the voltage at the emitter follows the input voltage. The voltage gain is less than unity but usually is close to unity ( $r_e$  is quite small, usually much smaller than  $R_e$ ).

The signal analysis can be performed directly on the circuit – that is, with the equivalent circuit implicitly assumed.
 
### Output Resistance

An alternative way of describing the performance of emitter follower is to specify the Thevenin equivalent circuit at the output. In the near figure it is represented the circuit used to compute the Thevenin output



resistance:  $R_o = \left. \frac{v_o}{i_o} \right|_{v_s=0}$  and the output resistance at the emitter lead:  $R_{oe} = \left. \frac{v_e}{i_{oe}} \right|_{v_s=0}$ .

The emitter voltage and current are:  $v_e (= v_o) = -i_b (R_s \parallel R_B + r_{be})$ ;  $i_e (= -i_{oe}) = (\beta + 1) \cdot i_b$ .


The output resistance on the emitter lead is: 
$$R_{oe} = \frac{-i_b(R_s \parallel R_B + r_{be})}{-(\beta+1) \cdot i_b} = \frac{R_s \parallel R_B + r_{be}}{\beta+1}$$

All resistances on the base side may be reflected to the emitter side after dividing their value by the factor  $(\beta+1)$  – that is **the reflection rule from base to emitter**.

The voltage gain from source to emitter (without load) and the overall voltage gain are:

$$A_{vs} = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = \frac{R_E}{R_E + r_e} \frac{R_i}{R_i + R_s}, \quad A_{vs} = A_{v0} \frac{R_L}{R_L + R_o}$$

 
The overall voltage gain was computed with the Thevenin equivalent of the voltage follower.


 
## Applications

**S7 – P1.** The transistor in the circuit of figure has  $\beta=100$  and  $V_{BE}=0.7\text{ V}$ .

- Find the dc voltages at the base, emitter and collector;
- Find  $g_m$  and  $r_{be}$  (assume  $V_T=25\text{ mV}$ ).
- If terminal Z is connected to ground, X connected to signal source  $v_i$ , and Y to an  $8\text{ k}\Omega$  load resistance, use the small signal model to find the voltage gain  $A_v = v_y / v_i$  (CE configuration).
- If Y is connected to ground, X to an input to signal source  $v_i$ , and Z to a load resistance of  $1\text{ k}\Omega$ , find the voltage gain  $A_v = v_z / v_i$  (CC configuration – voltage follower).
- If X is connected to ground, Z to an input signal source  $v_i$ , and Y to a load resistance of  $8\text{ k}\Omega$ , find the voltage gain  $A_v = v_y / v_i$  (common-base configuration).



$$a) I_C \cong I_E = 1\text{ mA}, \quad I_B = \frac{I_C}{\beta} = 0.01\text{ mA}, \quad V_B = -R_B I_B = -10\text{ k}\Omega \cdot 0.01\text{ mA} = -0.1\text{ V},$$


$$V_C = V_{CC} - R_C I_C = 10 - 8\text{ k}\Omega \cdot 1\text{ mA} = 2\text{ V}, \quad V_E = V_B - V_{BE} = -0.1 - 0.7 = -0.8\text{ V}.$$

$$b) g_m = \frac{I_C}{V_T} = \frac{I_C}{25\text{ mV}} = 40 I_C = 40 \cdot 1\text{ mA} = 40\text{ mA/V}; \quad r_{be} = \frac{\beta}{g_m} = \frac{100}{40\text{ mA/V}} = 2.5\text{ k}\Omega.$$

$$c) v_y = -i_c \cdot (R_C \parallel R_L) = -g_m v_{be} R_C; \quad v_i = v_{be} \text{ and}$$

$$A_v = \frac{v_y}{v_i} = -g_m R_C = -40\text{ mA/V} \cdot 4\text{ k}\Omega = -160$$

 
(with  $R_c = R_C \parallel R_L = 8\text{ k}\Omega \parallel 8\text{ k}\Omega = 4\text{ k}\Omega$ ).



$$d) v_i = i_e r_e + i_e R_L = i_e (r_e + R_L); \quad v_z = i_e R_L \text{ and}$$

$$A_v = \frac{v_z}{v_i} = \frac{R_L}{R_L + r_e} = \frac{1\text{ k}\Omega}{1\text{ k}\Omega + 25\Omega} = 0.976 \text{ (with } r_e = \frac{V_T}{I_C} = \frac{1}{40\text{ mA/V}} = 25\Omega\text{)}.$$
 
$$e) A_v = \frac{v_y}{v_i} = g_m R_C = 40\text{ mA/V} \cdot 4\text{ k}\Omega = 160.$$




**S7 – P2.** a) Determine the voltage gain and the input and output resistances for the amplifier in figure; consider:  $I_C = 2 \text{ mA}$ ,  $\beta = 200$ ,  $V_T = 25 \text{ mV}$ , ( $V_{BE} = 0.7 \text{ V}$ ).

b) Assume that a  $600 \Omega$ ,  $10 \text{ mV}$  (rms) voltage source is driving the amplifier and a  $2 \text{ k}\Omega$  load is connected at the output. Determine the overall gain and the output rms voltage.

c) If the emitter capacitor opens, what is the new value of voltage gain and the overall gain (point b conditions).

 d) Redesign the circuit with an additional resistance in the emitter to get a voltage gain of 10 (for no load conditions) keeping the same Q point.



Find the voltages at all nodes and the currents through all branches in the circuit for.

$$a) V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{4.7k}{24.7k} 9 = 1.7 \text{ V}, \quad I_E = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E} = \frac{1}{0.5k} = 2 \text{ mA},$$

$$I_B = \frac{I_E}{\beta} = 0.01 \text{ mA} \ll I_{Div} = 0.36 \text{ mA}, \quad V_{CE} = V_{CC} - R_C I_C - V_E = 9 - 4 - 1 = 4 \text{ V}.$$

$$\text{Transistor parameters are: } g_m = \frac{I_C}{V_T} = 40 I_C = 80 \text{ mA/V}; \quad r_{be} = \frac{\beta}{g_m} = \frac{200}{80m} = 2.5 \text{ k}\Omega.$$

$$\text{Amplifier parameters are: } A_{v0} = -g_m R_C = -80m \cdot 2k = -160; \quad R_o = R_C = 2 \text{ k}\Omega;$$

$$R_B = R_1 \parallel R_2 = 20k \parallel 4.7k = 3.2 \text{ k}\Omega, \quad R_i = R_B \parallel r_{be} = 3.2k \parallel 2.5k = 1.4 \text{ k}\Omega.$$

$$b) V_i = \frac{R_i}{R_i + R_s} V_s = \frac{1.4k}{1.4k + 0.6k} 10 \text{ mV} = 7 \text{ mV}; \quad V_o = |A_{v0}| \cdot V_i \frac{R_L}{R_L + R_o}; \quad A_v = \frac{V_o}{V_i} = A_{v0} \frac{R_L}{R_L + R_o};$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s} = A_{v0} \frac{R_L}{R_L + R_o} \frac{R_i}{R_i + R_s} = -160 \frac{2k}{2k + 2k} \frac{1.4k}{1.4k + 0.6k} = -56; \quad V_o = V_s |A_{vs}| = 560 \text{ mV};$$

$$V_o = V_s |A_{vs}| = 10 \text{ mV} \cdot 56 = 560 \text{ mV}; \quad \text{or} \quad V_o = V_i |A_v| = 7 \text{ mV} \cdot 160 \cdot \frac{2k}{2k + 2k} = 7 \text{ mV} \cdot 80 = 560 \text{ mV}.$$

$$c) A_{v0} = -\frac{R_C}{R_E + r_e} = -\frac{2k}{500 + 12.5} = -3.9, \quad (\text{with } r_e = 1/g_m = 1/80m = 12.5 \Omega);$$


$$R_{ib} = r_{be} + (\beta + 1)R_E = 2.5k + 201 \cdot 0.5k = 103 \text{ k}\Omega; \quad R_i = R_B \parallel R_{ib} = 3.2k \parallel 103k = 3 \text{ k}\Omega;$$

$$A_{vs} = A_{v0} \frac{R_L}{R_L + R_o} \frac{R_i}{R_i + R_s} = -3.9 \frac{2k}{2k + 2k} \frac{3k}{3k + 0.6k} = -3.9 \cdot 0.5 \cdot 0.83 = -1.62 \quad (34.6 \text{ time lower}).$$

d) Split the emitter resistance in two parts (see figure), one bypassed by the emitter capacitor ( $R_{E1}$ ) and one unbypassed ( $R_{E2}$ ); their sum should be equal to the previous emitter resistance to keep the same Q point. The unbypassed part gives the gain:

$$|A_{v0}| \cong \frac{R_C}{R_{E1}} = 10; \quad R_{E1} \cong \frac{R_C}{|A_{v0}|} = \frac{2k}{10} = 200 \Omega;$$
 
$$R_{E2} = R_E - R_{E1} = 500 - 200 = 300 \Omega.$$




**S8 – P1.** a) Calculate the voltage gain from base to collector for the amplifier shown in figure. If the ac source signal is a sine wave with 0,1 V peak, what does  $\hat{V}_c$  equal? And  $\hat{V}_e$ ? (Assume  $V_{EB}=0.7\text{ V}$  and  $V_T=25\text{ mV}$ .)

b) If the collector coupling capacitor opens, what is the new value of voltage gain (from base to collector)?

c) If the collector capacitor shorts what effect will have on the dc operation and on the ac operation?

 d) If the base coupling capacitor shorts what will do this to the dc operation (assume  $V_{ECsat}=0.3\text{ V}$ ).



a) dc analysis: 
$$V_{R2} \cong \frac{R_2}{R_1 + R_2} V_{EE} = \frac{20k}{20k + 47k} 20 = 6\text{ V},$$

$$I_E = \frac{V_{R_E}}{R_E} = \frac{V_{R2} - V_{EB}}{R_E} = \frac{5.3}{4.18k} = 1.27\text{ mA}, \quad \left( I_{R2} = \frac{V_E}{R_1 + R_2} = 0.3\text{ mA} = 0.24 I_E \right),$$

$$V_{EC} = V_{EE} - V_{R_E} - R_C I_C = 20 - 5.3 - 6k \cdot 1.27\text{ m} = 7.1\text{ V} \text{ (BJT is in the active regime).}$$


Transistor parameters are: 
$$r_e = \frac{V_T}{I_C} = \frac{25\text{ m}}{1.27\text{ m}} \cong 20\Omega; \quad \alpha \cong 1.$$

ac analysis: 
$$v_b = i_e (r_e + R_{E1})$$

$$v_c = -i_c (R_C \parallel R_L) \cong -i_e (R_C \parallel R_L);$$

$$\hat{V}_c = \left| \frac{-i_c (R_C \parallel R_L)}{i_e (r_e + R_{E1})} \right| \cdot \hat{V}_b = \frac{R_C \parallel R_L}{r_e + R_{E1}} \cdot \hat{V}_b = \frac{2k}{20 + 180} 0.1 = 1\text{ V}.$$
 
$$\hat{V}_e = \frac{R_{E1}}{r_e + R_{E1}} \cdot \hat{V}_b = \frac{180}{20 + 180} 0.1 = 0.09\text{ V}.$$



b)  $R_L$  is an open-circuit (w/o  $R_L$ ): 
$$A_{v0} = \frac{v_c}{v_b} = -\frac{R_C}{r_e + R_{E1}} = -\frac{6k}{20 + 180} = -30.$$

c) dc analysis ( $R_L$  is in parallel with  $R_C$ ): 
$$V_C = I_C (R_C \parallel R_L) = 1.27\text{ m} \cdot 2k = 2.54\text{ V},$$

$$V_{EC} = V_{EE} - V_{R_E} - V_C = 20 - 2.54 - 5.3 = 12.2\text{ V}; \text{ instead of } 7.1\text{ V}; \text{ ac operation is the same.}$$

d) dc analysis: 
$$V_B = 0; \quad V_E = V_{EB} = 0.7\text{ V}, \quad \text{For the transistor in active regime,}$$

the emitter current would be: 
$$I_E = \frac{V_{EE} - V_E}{R_E} = \frac{19.3}{4.18k} = 4.6\text{ mA}.$$

The maximum possible collector current is: 
$$I_{C\text{max}} = \frac{V_{EE}}{R_E + R_C} = \frac{20}{4.18k + 6k} = 1.96\text{ mA};$$

(with the transistor in saturation; between active mode and saturation mode). Because  $I_E > I_{C\text{max}}$  the transistor is in saturation and  $V_{EC} = V_{ECsat} = 0.3\text{ V}$ ;


The collector current is: 
$$I_C = \frac{V_C}{R_C} = \frac{V_E - V_{ECsat}}{R_C} = \frac{0.7 - 0.3}{6k} = 0.067\text{ mA}.$$

The base current is: 
$$I_B = I_E - I_C = 4.6\text{ m} - 0.67\text{ m} \cong 3.9\text{ mA}.$$

**S8 – P2.** For the emitter follower circuit shown in figure, the BJT is specified to have  $\beta$  values in the range of 100 to 500 and  $V_{BE}=0.7$  V.

For the two extreme value of  $\beta$  find:

 - The bias point:  $I_E$  and  $V_E$ ;
- The input resistance  $R_i$ ;
- The overall voltage gain  $A_{vs} = v_o / v_s$ .



$$a) I_E = \frac{V_{CC} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} = \frac{9 - 0.7}{1k + \frac{100k}{101 \dots 501}} = (4.17 \dots 6.92) \text{ mA},$$

$$V_E = R_E I_E = (4.17 \dots 6.92) \text{ V}.$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ m}}{(4.17 \dots 6.92) \text{ m}} = (6 \dots 3.6) \Omega;$$

$$b) R_{ib} = (\beta + 1) \cdot (r_e + R_E \parallel R_L) = (101 \dots 501) \cdot (6 \dots 3.6 + 500) = 51 \dots 252 \text{ k}\Omega;$$

$$R_i = R_B \parallel R_{ib} = 33.8 \dots 71.6 \text{ k}\Omega.$$

$$c) R_e = R_E \parallel R_L = 500 \Omega; \quad A_{vs} = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = \frac{R_e}{R_e + r_e} \frac{R_i}{R_i + R_s} = \frac{1}{1 + \frac{r_e}{R_e}} \cdot \frac{1}{1 + \frac{R_s}{R_i}};$$

$$A_{vs} = \frac{1}{1 + \frac{6 \dots 3.6}{500}} \cdot \frac{1}{1 + \frac{10k}{(33.8 \dots 71.6)k}} = (0.988 \dots 0.993) \cdot (0.77 \dots 0.877) = 0.76 \dots 0.87.$$