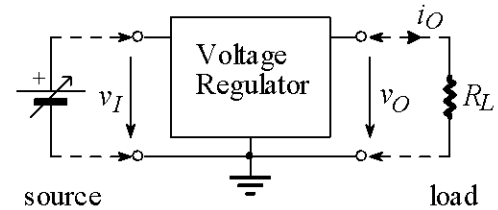


## Voltage Regulators

The purpose of a voltage regulator is to provide a constant dc output that is practically independent on the variations of: the input voltage, output load current and temperature. In Romanian the circuit is called "Stabilizator de tensiune"

The two fundamental classes of voltage regulators are:

- linear regulators and
- switching regulators.



### Voltage Regulators Parameters

The two basic aspects of voltage regulation are: line regulation and load regulation.

**Line regulation** can be defined as the percentage change in the output voltage for one volt change in the input (line) voltage (measured in %/V):  $LineRg = \frac{\Delta v_O}{V_O} \cdot \frac{100}{\Delta v_I}$ .

**Load regulation** can be defined as the percentage change in output voltage for a given change in current (e.g. from no-load "NL" to full-load "FL"):  $LoadRg = \frac{V_{NL} - V_{FL}}{V_{FL}} \cdot 100$ .

**For small variations** of the output voltage the differentials can be used and:

$$dv_O = \frac{dv_I}{S} - R_o \cdot di_O + TC \cdot dT.$$

From this equation, the parameters of the voltage regulator can be found:

$S = \left. \frac{dv_I}{dv_O} \right|_{di_O, dT=0}$  - The  $S$  factor, regulation coefficient (Romanian: coeficient de stabilizare);

$R_o = - \left. \frac{dv_O}{di_O} \right|_{dv_I, dT=0}$  - The output resistance (or internal resistance of the source);

$TC = \left. \frac{dv_O}{dT} \right|_{dv_I, dv_O=0}$  - The thermal coefficient, (Romanian:  $S_T$ , coeficient de temperatură).

The small variation parameters of the regulator can be computed using the small signal equivalent circuit.


### Linear Regulators

There are two basic types of linear regulators: series regulator and shunt regulator.

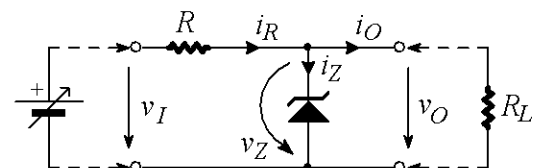
#### The Zener Diode Voltage Regulator

This is the simpler shunt regulator; it consists on a Zener diode in parallel with the load and a series resistor (between input and output).

Input voltage variations and output current variations are converted by the circuit in Zener current variations. As long as:  $I_{Zmin} < i_Z < I_{Zmax}$ , the Zener voltage is almost constant:  $v_Z = ct = V_Z$  and  $v_O = v_Z = ct$ .



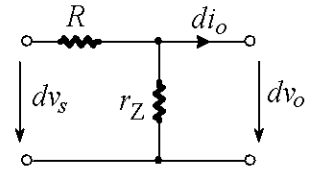The small variation parameters of the voltage the regulator are computed based on the small signal equivalent circuit, where the Zener diode is replaced by its dynamic resistance:



$$S = \left. \frac{dv_I}{dv_O} \right|_{di_O=0} = \frac{R+r_Z}{r_Z} \cong \frac{R}{r_Z} \text{ (the voltage divider rule);}$$


$$R_o = - \left. \frac{dv_O}{di_O} \right|_{dv_I=0} = r_Z \parallel R \cong r_Z; \text{ the approximations are correct for the usual case: } r_Z \ll R.$$

The output resistance of the voltage regulator depends directly on the dynamic resistance of the Zener diode (de aceea în română circuitul se numește “Stabilizator parametric”).
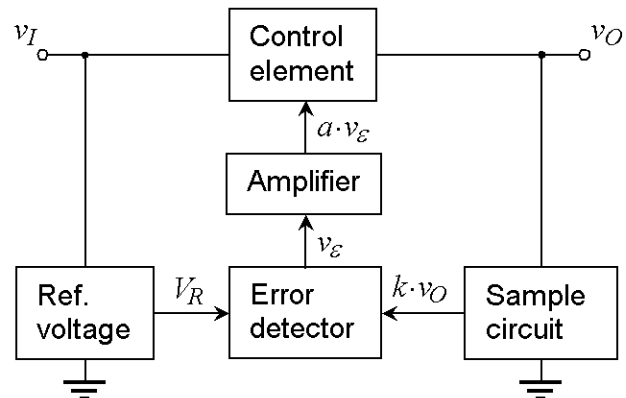
### The Series Voltage Regulator

The control element is in series with the load; between input and output. The sample circuit senses a change in the output voltage. The error detector compares the sampled voltage with a reference voltage and causes the control element to compensate in order to maintain a constant output voltage:

$$v_\varepsilon = V_R - k \cdot v_O = 0 \text{ and } v_O = V_R / k = \text{ct.}$$



### The Emitter-Follower Series Regulator

The simplest series regulator consists on an emitter-follower and a Zener diode regulator (that provides the reference voltage). The circuit is presented in the next figure.

The output voltage is constant:  $v_O = V_Z - V_{BE} = \text{ct.}$

The emitter follower reduces the output current variation


$$\text{by a factor of } \beta: \Delta i_Z = \frac{-\Delta i_O}{\beta}.$$

The load current pass through the series transistor, the voltage across the series transistor is:  $v_{CE} = v_I - v_O$  and

the power dissipation is:  $P_D = v_{CE} \cdot i_E = (v_I - v_O) \cdot i_O$ .

Q is a power transistor and it is often used with a heatsink.

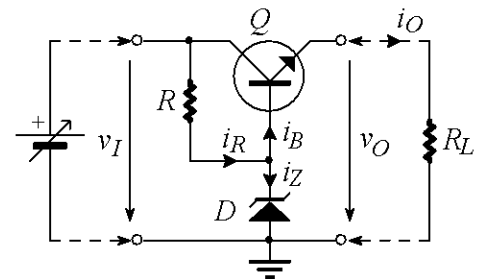
The regulator parameters can be found from the small-signal equivalent circuit:



$$S = \left. \frac{dv_I}{dv_O} \right|_{di_O=0} = \frac{v_i}{v_o} \Big|_{i_o=0} = \frac{R+r_Z}{r_Z} \cong \frac{R}{r_Z};$$

$$R_o = - \left. \frac{dv_O}{di_O} \right|_{dv_I=0} = - \frac{v_o}{i_o} \Big|_{v_i=0} = \frac{(r_{be} + R \parallel r_Z) \cdot i_b}{(\beta + 1) \cdot i_b} \cong \frac{r_{be} + r_Z}{\beta + 1} = \frac{1}{g_m} + \frac{r_Z}{\beta}.$$

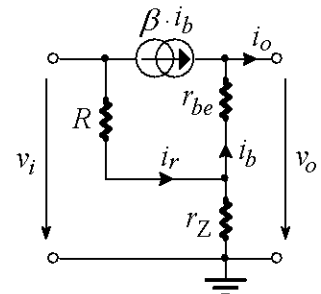The  $S$  factor can be much greater than that of the zener regulator, because  $R$  can be much greater, being passed by the Zener current, that is much lower than the output current.



The output resistance is much smaller than for the zener regulator, the dynamic resistance of the zener being reduced by the high  $\beta$  factor (and  $1/g_m = r_e$  has a very low value).


### The Basic Op Amp Series Regulator

The reference voltage  $V_R$  is the input of the noninverting amplifier and the  $R_1/R_2$  voltage divider forms the negative feedback network. The ideal closed loop gain is:

$$A = 1 + \frac{R_2}{R_1}.$$

Therefore the regulated voltage is a constant value determined by the Zener voltage and

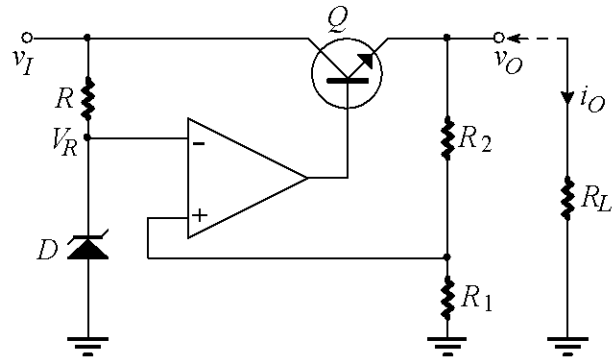the resistor ratio:  $v_O = \left(1 + \frac{R_2}{R_1}\right) \cdot V_R.$




### The Short-Circuit or Overload Protection

If an excessive amount of load (output) current is drawn, the series-pass transistor  $Q_1$  can be quickly destroyed. One method of current limiting to prevent overloads is the “constant current limiting”; it consists of transistor  $Q_2$  and resistor  $R_3$  of the circuit in the next figure.

The voltage load through  $R_3$  creates a voltage from base to emitter of  $Q_2$ . For normal load current the voltage drop across  $R_3$  is small and  $Q_2$  is off. When  $i_O$  reaches the limiting value, the voltage drop across  $R_3$  is sufficient to turn on  $Q_2$ . Enough  $Q_1$  base current is diverted into  $Q_2$  so that  $i_O$  is limited to its maximum value:

$$I_{O\max} \cong \frac{V_D}{R_3} = \frac{0.7}{R_3}.$$

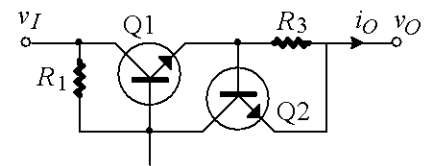
Since  $v_{BE}$  voltage is limited to about 0.7 V for a silicon transistor, the voltage drop across  $R_3$  is held to this value and the load current is limited to  $I_{O\max}$ .



### Application

#### VR – P1.

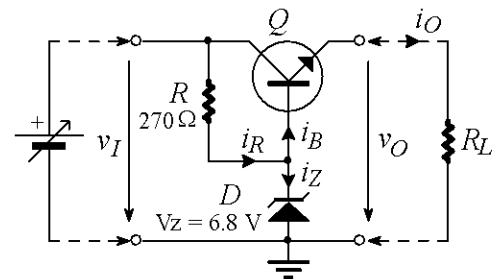1. In the next figure consider  $V_I = 10 \text{ V}$  and  $V_{BE} = 0.7 \text{ V}$ . What is  $v_O$ ?
2. If  $\beta = 50$  and  $R_L = 22 \Omega$  what is the base current and the zener current for  $V_I = 10 \text{ V}$ ?
3. If  $v_I$  varies from 10 to 15 V and  $R_L$  varies from  $22 \Omega$  to  $500 \Omega$  what is the maximum power dissipation in the transistor, in the Zener and in  $R$ ?
4.  $R_L$  changes from  $22 \Omega$  to  $500 \Omega$ . If  $\beta = 50$  and  $r_Z = 5 \Omega$ , what is the approximate change in output voltage and the load regulation (expressed in %)?



1.  $V_O = V_Z - V_{BE} = 6.8 - 0.7 = 6.1 \text{ V}$ .

2.  $i_R = i_Z + i_B$ .  $i_Z = i_R - i_B = \frac{v_I - V_Z}{R} - \frac{i_O}{\beta} = 11.9 \text{ m} - 5.5 \text{ m} = 6.4 \text{ mA}$ ;

$$i_O = \frac{10 - 6.1}{270} = 11.9 \text{ mA}, \quad i_O = \frac{V_O}{R_L} = \frac{6.1}{22} = 0.277 \text{ A} = 277 \text{ mA}, \quad i_B = \frac{i_O}{\beta} = \frac{277 \text{ m}}{50} = 5.5 \text{ mA}.$$

3. The transistor power dissipation is:  $P_{dQ} = v_{CE} \cdot i_E = (v_I - V_O) \cdot i_O$ ;

Its maximum power dissipation is:  $P_{dQM} = (v_{IM} - V_O) \cdot i_{OM} = (15 - 6.1) \cdot 0.277 = 2.47 \text{ W}$ .

The zener diode power dissipation is:  $P_{dZ} = V_Z \cdot i_Z \cong V_Z \cdot \left( \frac{v_I - V_Z}{R} - \frac{i_O}{\beta} \right)$ ; its maximum is:

$$P_{dZM} = V_Z \cdot \left( \frac{v_{IM} - V_Z}{R} - \frac{V_O}{\beta \cdot R_{LM}} \right) = 6.8 \cdot \left( \frac{15 - 6.8}{270} - \frac{6.1}{50 \cdot 500} \right) = 0.207 \text{ W}.$$

The resistance power dissipation is:  $P_{dR} = \frac{(v_I - V_Z)^2}{R}$ ;

Its maximum power dissipation is:  $P_{dRM} = \frac{(v_{IM} - V_Z)^2}{R} = \frac{(15 - 6.8)^2}{270} = 0.25 \text{ W}$ .

4. With  $V_{BE} = \text{ct}$ , the output voltage  $v_O$  is modified because of  $v_Z$  variation (produced by  $i_Z$  variation). To simplify the computing we will consider a constant  $v_Z (= V_Z)$  when computing the zener current variation,  $\Delta i_Z$ . The limits of the zener current are given by the limits of the output current (load resistance limits); the minimum zener current has been computed for the maximum load current (minimum load resistance) at point 2. The maximum zener current results for the minimum load current (maximum load resistance):

$$i_{Z \max} = \frac{v_I - V_Z}{R} - \frac{i_{O \min}}{\beta} = i_R - \frac{V_O}{\beta \cdot R_{L \max}} = 11.9 \text{ m} - \frac{6.1}{50 \cdot 500} = 11.9 \text{ m} - 502 \text{ m} = 11.7 \text{ mA},$$

$$\Delta v_Z = r_Z \cdot \Delta i_Z = 5 \cdot (11.7 - 6.4) \text{ m} = 26.5 \text{ mV}. \quad \text{LoadRg} = \frac{\Delta v_O}{V_O} 100 = \frac{26.5 \text{ m}}{6.1} 100 = 0.43\%.$$