

## Partial 2 – Dispozitive Electronice

### 11.01.2019

#### Rezolvare problema

- a) M1 – conexiune DC deoarece in - G, out - S  
M2 – conexiune SC deoarece in – G, out - D
- b) PSF
  - M1 - TEC-MOS canal inițial

$$\left. \begin{array}{l} V_{GS1} = V_{G1} - V_{S1} \\ V_{G1} = 0 \\ V_{S1} = I_{D1}R_2 = 6I_{D1} \end{array} \right\} \Rightarrow V_{GS1} = -6I_{D1}$$

$$I_{D1} = I_{DSS} \left( 1 - \frac{V_{GS1}}{V_{GS(off)}} \right)^2 = 5 \left( 1 - \frac{-6I_{D1}}{-2} \right)^2 = 5(1 - 3I_{D1})^2$$

$$I_{D1} = 5(1 - 6I_{D1} + 9I_{D1}^2) = 5 - 30I_{D1} + 45I_{D1}^2$$

$$45I_{D1}^2 - 31I_{D1} + 5 = 0$$

$$I_{D1(1,2)} = \frac{31 \pm \sqrt{31^2 - 4 \cdot 45 \cdot 5}}{90} = \frac{31 \pm 7,8}{90} \Rightarrow \begin{cases} I_{D1(1)} = \frac{31 + 7,8}{90} = 0,43mA \\ I_{D1(2)} = \frac{31 - 7,8}{90} = 0,26mA \end{cases}$$

$$V_{GS1(1)} = -6 \cdot 0,43 = -2,58V$$

$$V_{GS1(2)} = -6 \cdot 0,26 = -1,56V \rightarrow |-1,56| < |-2| \Rightarrow I_{D1} = 0,26mA$$

$$TIIK : V_{DD} = I_{D1}R_2 + V_{DS1} + I_{D1}R_3 \Rightarrow V_{DS1} = V_{DD} - I_{D1}(R_2 + R_3) = 18V - (0,26mA)(9k\Omega) = 15,66V$$

$$PSF_{J1(M1)} = \begin{cases} V_{GS1} = -1,56V \\ I_{D1} = 0,26mA \\ V_{DS1} = 15,66V \end{cases}$$

- M2 - TEC-MOS canal induș

$$I_{D(on)} = K(V_{GS} - V_{GS(th)})^2 \Rightarrow K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{324mA}{(10-1)^2V^2} = 4mA/V^2$$

$$\left. \begin{array}{l} V_{GS2} = V_{G2} - V_{S2} \\ V_{G2} = \frac{R_5}{R_4 + R_5} V_{DD} = \frac{1M}{9M} 18V = 2V \\ V_{S2} = 0 \end{array} \right\} \Rightarrow V_{GS2} = V_{G2} = 2V$$

$$I_{D2} = K(V_{GS2} - V_{GS(th)})^2 = 4(2-1)^2 = 4mA$$

$$TIIK : V_{DD} = I_{D2}R_6 + V_{DS2} \Rightarrow V_{DS2} = V_{DD} - I_{D2}R_6 = 18V - (4mA)(2k\Omega) = 10V$$

$$PSF_{M1(M2)} = \begin{cases} V_{GS2} = 2V \\ I_{D2} = 4mA \\ V_{DS2} = 10V \end{cases}$$

- c) Parametrii de s.m.


$$g_{m1} = \frac{2I_{DSS}}{|V_{GS(off)}|} \left( 1 - \frac{V_{GS1}}{V_{GS(off)}} \right) = \frac{2 \cdot 5}{2} \left( 1 - \frac{-1,56}{-2} \right) = 1,1mS$$

$$g_{m2} = 2K(V_{GS2} - V_{GS(th)}) = 2 \times 4 \times (2-1) = 8mS$$

$$V_{DS1} > (V_{GS1} - V_{GS(off)}) = -1,56 - (-2) = 0,44V, 15,66V > 0,44V$$

$$V_{DS2} \geq (V_{GS2} - V_{GS(th)}) = 2V - 1V = 1V ; 10V > 1V$$

d)  $A_v$

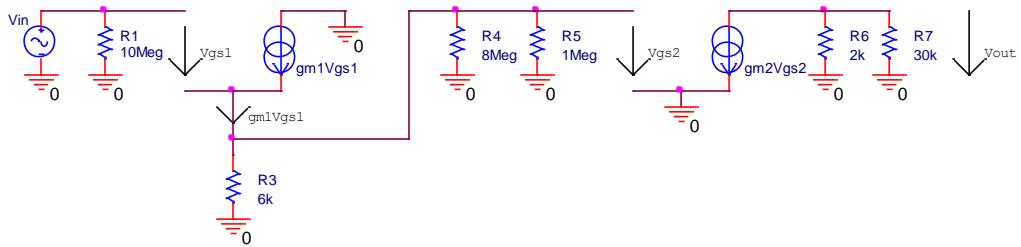

Schema de semnal mic

$$A_v = \frac{V_{out}}{V_{in}}$$

$$V_{out} = -g_{m2}v_{gs2}(R_6\|R_7)$$

$$g_{m1}v_{gs1}(R_3\|R_4\|R_5) = v_{gs2}$$

$$V_{in} = v_{gs1} + g_{m1}v_{gs1}(R_3\|R_4\|R_5) \Rightarrow v_{gs1} = \frac{V_{in}}{1 + g_{m1}(R_3\|R_4\|R_5)}$$

$$A_v = -g_{m2}(R_6\|R_7) \times \frac{g_{m1}(R_3\|R_4\|R_5)}{1 + g_{m1}(R_3\|R_4\|R_5)}$$

$$R_6\|R_7 = \frac{2k \times 30k}{32k} = 1,875k$$

$$R_3\|R_4\|R_5 = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}} = \frac{1}{\frac{1}{6k} + \frac{1}{8M} + \frac{1}{1M}} = 5,96k\Omega$$

$$A_v = -(8mS)(1,875k\Omega) \times \frac{(1,1mS)(5,96k\Omega)}{1 + (1,1mS)(5,96k\Omega)} = -13$$